

LC L36-180A-480

LC L36-180A-480, Filter

Code: R732180070000

> Load current (A): 180

> Frequency (Hz): 60

> Q (kvar): 53,12

> cabinet: FR4

Description

LCL filters have been specially designed to eliminate the harmonics from the current absorbed by 6-pulse power converters, such as frequency variators for motors, UPS, etc. These are essentially passive filters based on a series-parallel combination of inductances and capacitors, adapted to filter the input of power converters.

Application

- Reduction of the current wave's distortion towards the network and the rest of the installation.
- Compliance with the **IEC 61000-3-4, IEC 61000-3-12, IEC 61800-3 and IEEE-519.**
- Energy savings with the reduction of the root mean square current (RMS), thus reducing the kV·A demand.
- Increase of the working life of units above this location with the corresponding reduction of thermal losses generated.
- Limits current transients, preventing damages caused to the converter and overvoltage trips that affect production processes.

Creation date: 22/11/2026 - CIRCUTOR, SAU reserves the right to make technical changes or modify the content/images of this document without prior notice, in order to improve its reliability, functionality, design or for other reasons.
It accepts no liability for any errors, inaccuracies or possible lack of information in this document.



LC L36-180A-480

Harmonic filter for power converters

Code: R732180070000

Specifications

AC power supply

Frequency	60 Hz
Nominal voltage	400 Vca /480 Vca F-F (otras tensiones, bajo demanda)

Mechanical characteristics

Size (mm) width x height x depth	800 x 1900 x 650 (mm)
Envelope	Treated and painted steel. Frame RAL 1013 / Doors RAL 3005
Fastening	On the ground

Environmental characteristics

Protection class	IP 20
Relative humidity (without condensation)	80%
Installation, location, position.	Inside
Operating temperature	+ 35 °C

Electrical characteristics

Nominal current voltage drop	< 2 %
LC load current (RMS)	180 A
Filtered current If (RMS)	72 A
Residual current THD	Approx. 8%

Current measurement circuit

Allowable overload	1,5 Ic (≤ 1 min.) + Ic (≤ 5 min.) (at maximum operating temperature)

Standards

Standards	UNE-EN 60439 , UNE-EN60831 , IEC 61000-6-3 , IEC 61000-6-4, Class A

LCL
Harmonic filters for power converters

CODE	TYPE	Load current (A)	Q (kvar)
400 V			
R73107.	LC L35-16A-400	16	3,27
460 - 480 V			
R732140070000	LC L36-76A-480	76	22,77
R732150070000	LC L36-90A-480	90	26,56
R732160070000	LC L36-110A-480	110	30,36
R732170070000	LC L36-150A-480	150	45,53

Creation date: 22/11/2026 - CIRCUTOR, SAU reserves the right to make technical changes or modify the content/images of this document without prior notice, in order to improve its reliability, functionality, design or for other reasons.
It accepts no liability for any errors, inaccuracies or possible lack of information in this document.



LC L36-180A-480

Harmonic filter for power converters

Code: R732180070000

CODE	TYPE	Load current (A)	Q (kvar)
R732180070000	LC L36-180A-480	180	53,12
R732190070000	LC L36-220A-480	220	60,71
R732200070000	LC L36-260A-480	260	68,3
R732210070000	LC L36-320A-480	320	91,07

Please contact us for other current, frequency and/or voltage values Optional: Overcompensation kit

Creation date: 22/11/2026 - CIRCUTOR, SAU reserves the right to make technical changes or modify the content/images of this document without prior notice, in order to improve its reliability, functionality, design or for other reasons.
It accepts no liability for any errors, inaccuracies or possible lack of information in this document.




LC L36-180A-480

Harmonic filter for power converters

Code: R732180070000

Connections

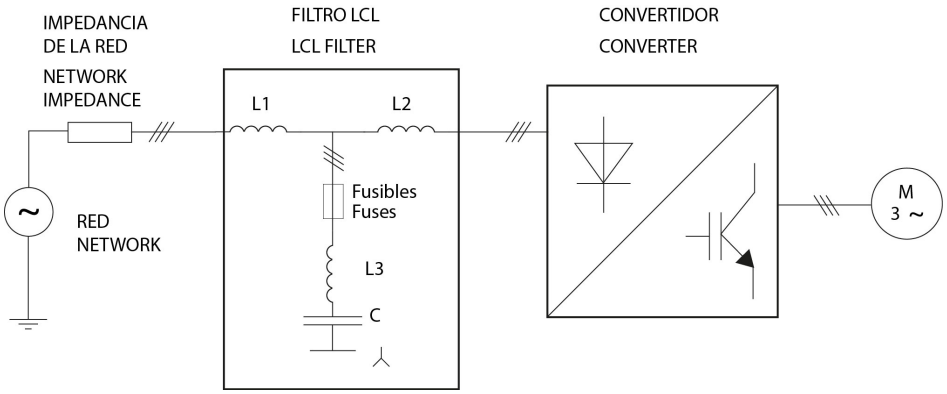

Creation date: 22/11/2026 - CIRCUTOR, SAU reserves the right to make technical changes or modify the content/images of this document without prior notice, in order to improve its reliability, functionality, design or for other reasons.
It accepts no liability for any errors, inaccuracies or possible lack of information in this document.